

CHALLENGING EXPERIMENT STATIC

CMOS CIRCUIT

AMIRTHA PRASAD

22BEC1002

AIM:

To draw a static CMOS circuit of given Boolean expressions and verify the truth table using transient analysis.

TOOLS:

Linux operated computing system, Cadence® Virtuoso, gpdK 180nm technology library.

PROCEDURE:

1. Consider the expressions $C = ((A + B) C_{in} + AB)$ and $S = ((A + B + C_{in}) C + ABC_{in})$ which are expressions of sum and carry of a full adder combinational circuit.
2. Draw a static CMOS diagram for the given expression using PMOS and NMOS.
3. Verify the truth table using transient analysis.
4. Calculate delay and power for Sum and carry.

SCREENSHOTS AND TABULAR COLUMN:

Delay calculation for sum:

Values	Input signal	Output signal	rise/fall	delay(ps)
001	Cin(1r)	Sum	rise	105.8
010	Cin(1f)	Sum	rise	88.11
111	Cin(2r)	Sum	rise	105.6
100	Cin(2f)	Sum	rise	88.08
011	B(1r)	Sum	fall	247.0
110	A(1r)	Sum	fall	137.4
101	B(1f)	Sum	fall	230.6
000	A(1f)	Sum	fall	119.4


1. For rising:
 - a) Best case delay: 88.08ps (100)
 - b) Worst case delay: 105.8ps (001)
2. For falling:
 - a) Best case delay: 119.4ps (000)
 - b) Worst case delay: 247.0ps (011)

Delay calculation for carry:


Values	Input signal	Output signal	rise/fall	delay(ps)
011	B(1r)	C	rise	196.3
110	A(1r)	C	rise	165.3
101	Cin(3r)	C	rise	198.1
111	B(4r)	C	rise	73.79
001	Cin(1r)	C	fall	80.07
010	Cin(1f)	C	fall	46.37
100	B(2f)	C	fall	75.11
000	Cin(4f)	C	fall	80.21

1. For rising:
 - a) Best case delay: 73.79ps (111)
 - b) Worst case delay: 198.1ps (101)
2. For falling:
 - a) Best case delay: 46.37ps (010)
 - b) Worst case delay: 80.21ps (000)


1. SCHEMATIC OF CMOS CIRCUIT:

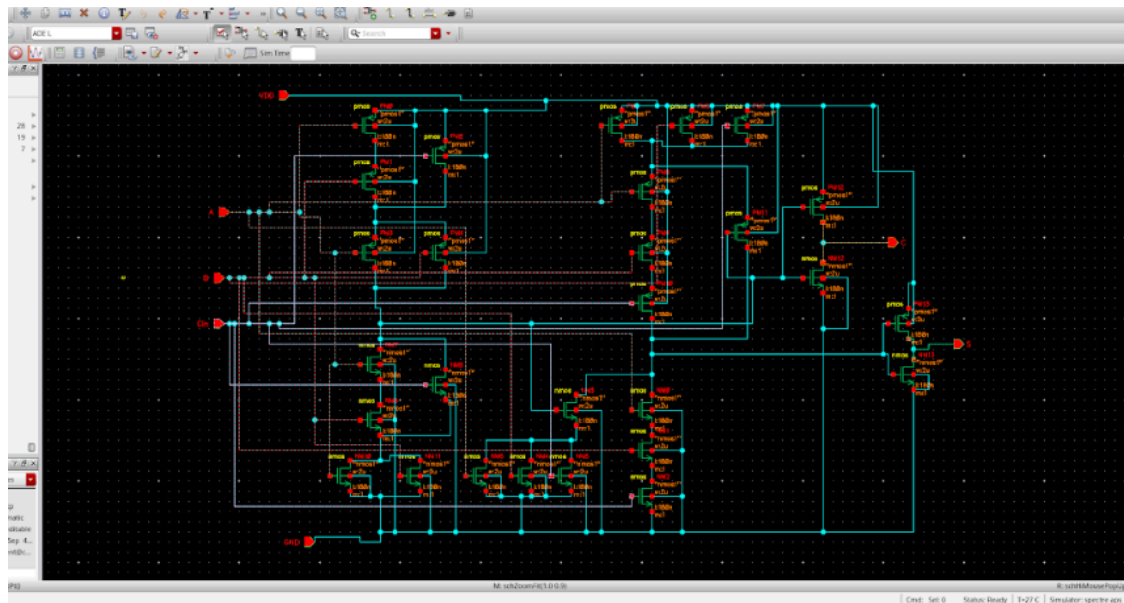

2. TRANSIENT ANALYSIS:

 

3. POWER CALCULATION:

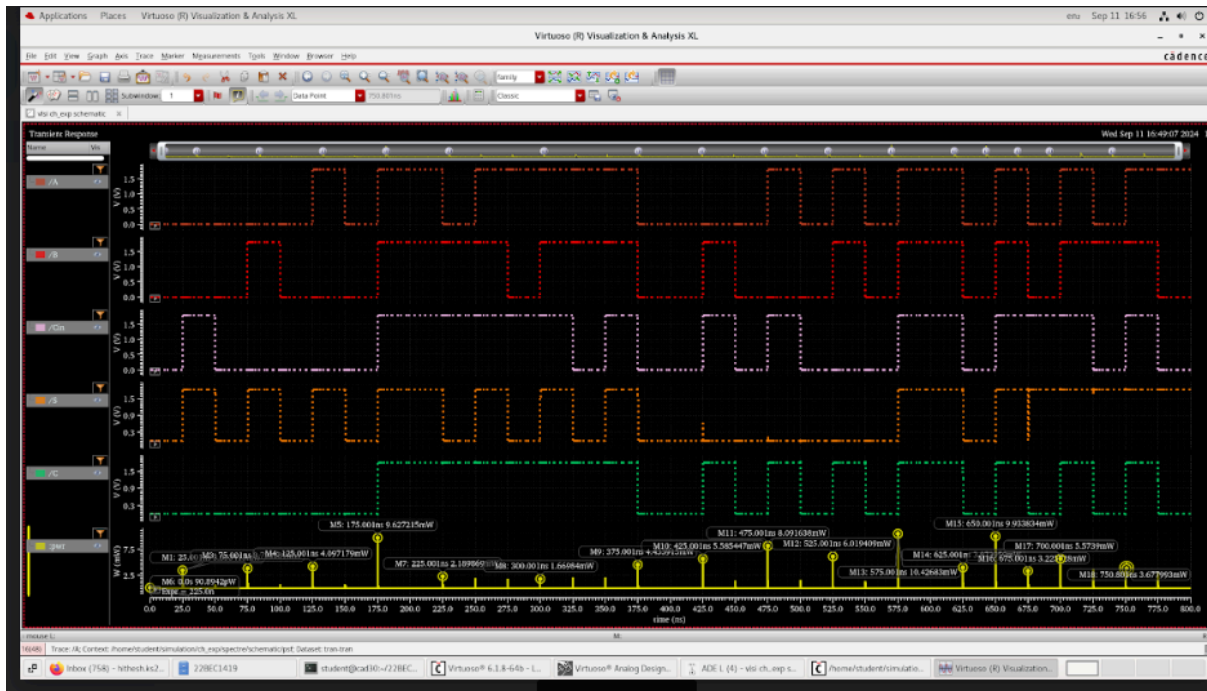

INFERENCE:

1. Truth table is verified by giving different input values for the variables for the combinational circuit.
2. The transient analysis is performed to verify the CMOS circuit.
3. The delay and power for sum and carry is calculated for all values and best and worst cases delay are analyzed.